

# Memory Elements (II)

*CS31*

*Pascal Van Hentenryck*




# Overview

## Memory Elements (II)

- registers
- register files

# The Big Picture

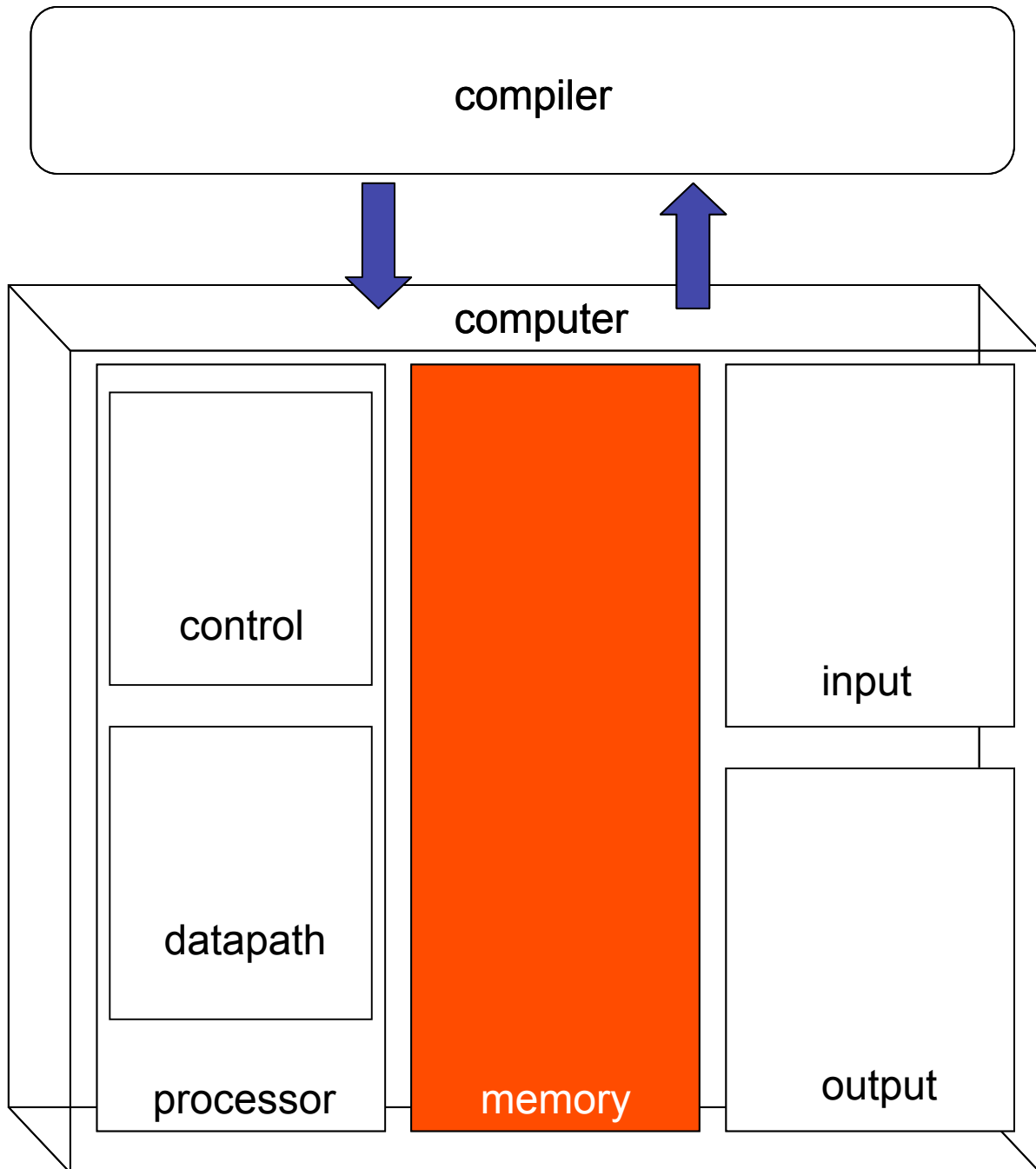

# Abstraction Hierarchy

**Programming Language**

**Assembly Language**

**Machine Language**


**Sequential Circuit**

**Combinational Circuit**

**Binary Value**

**Voltage**

# 2-bit Register

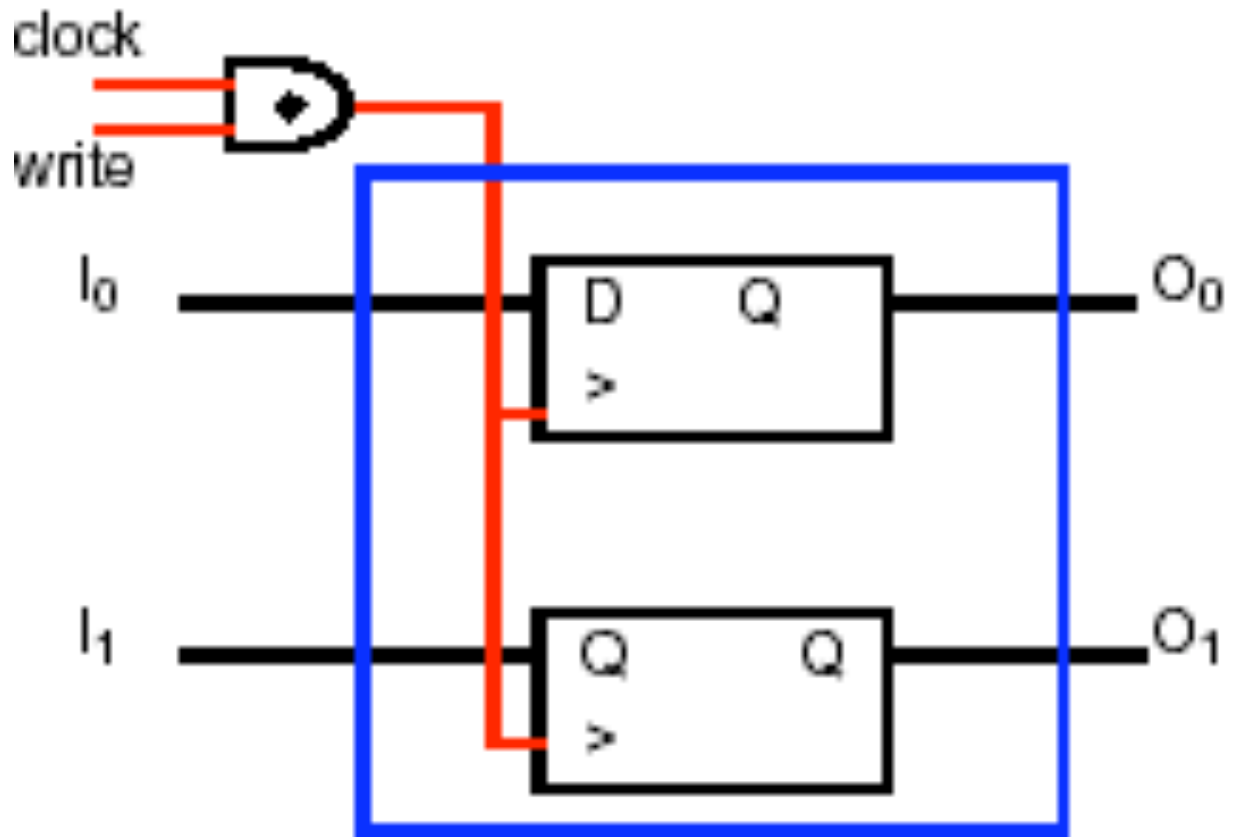


The register is written

- on the clock edge
- whenever the write signal is enabled

# Register Files

A register file is a set of registers

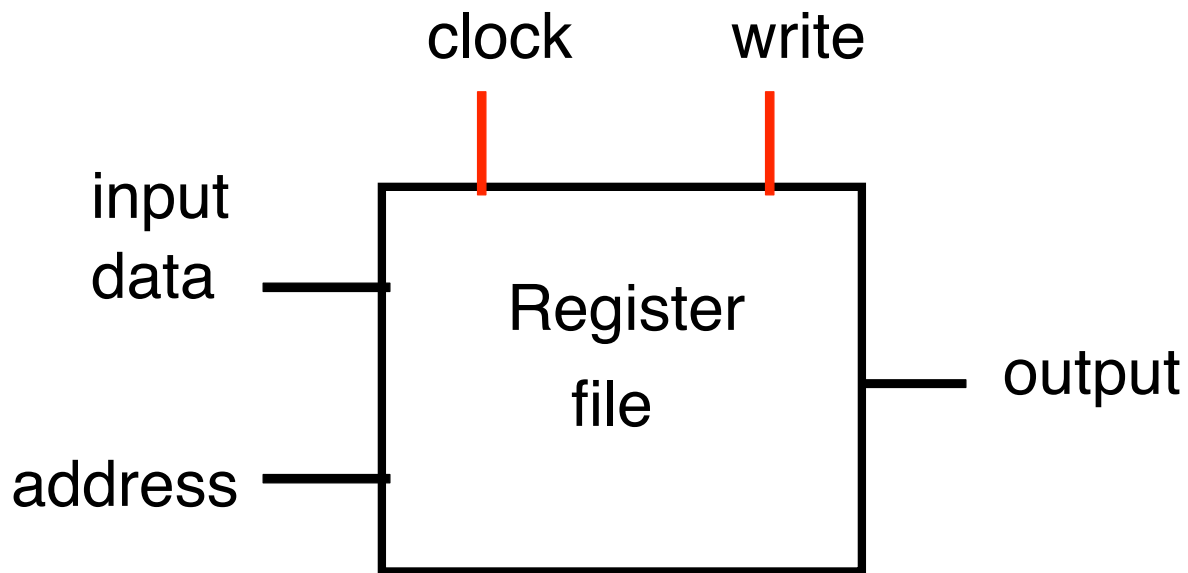


Construct a 4 register file with 8-bit registers

- size of address?  
2 bits addressing 4 registers
- size of input data?  
8-bits to write to the 8-bit registers
- size of output data?  
8-bits, also from the 8-bit registers

# 1-bit Register File

We want each register storing one bit

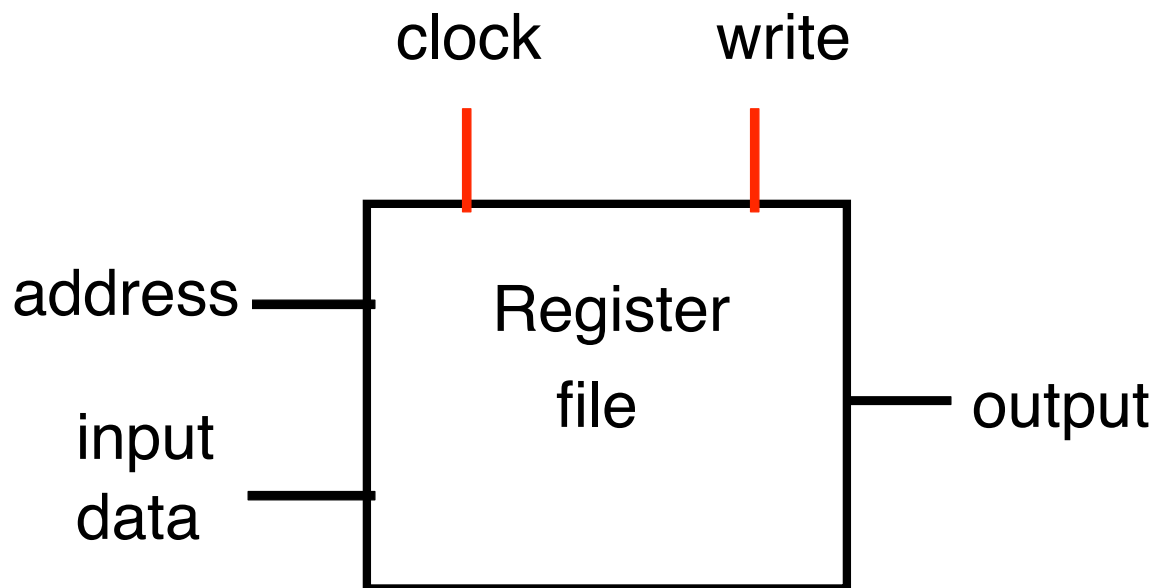


Proceed in two parts

- Read Part
- Write Part

# 1-bit Register File


We want each register storing one bit

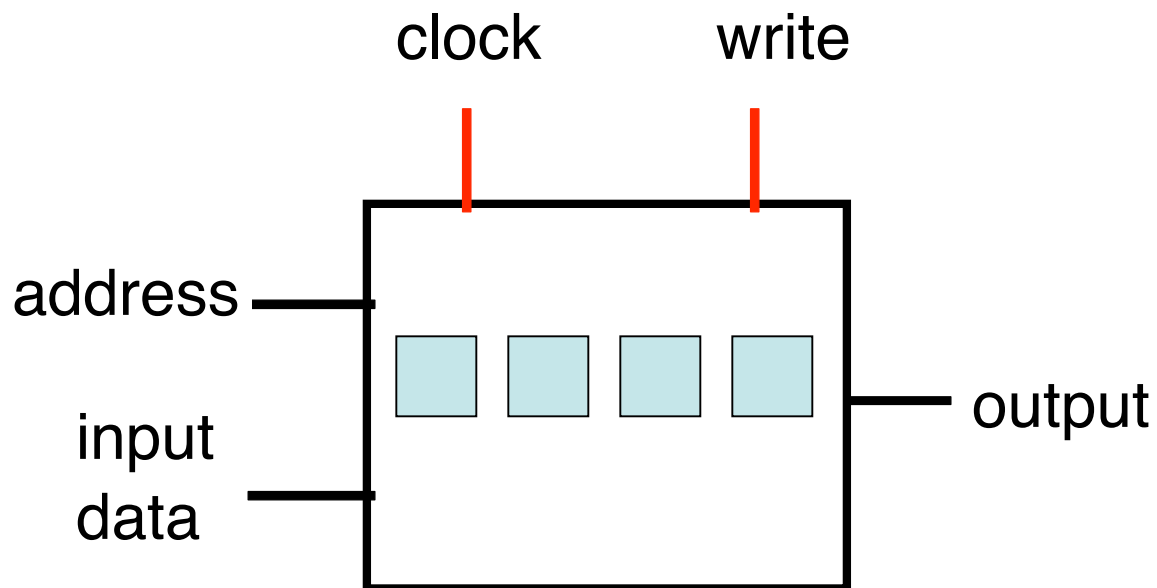


Proceed in two parts

- Read Part
- Write Part

# Read Part

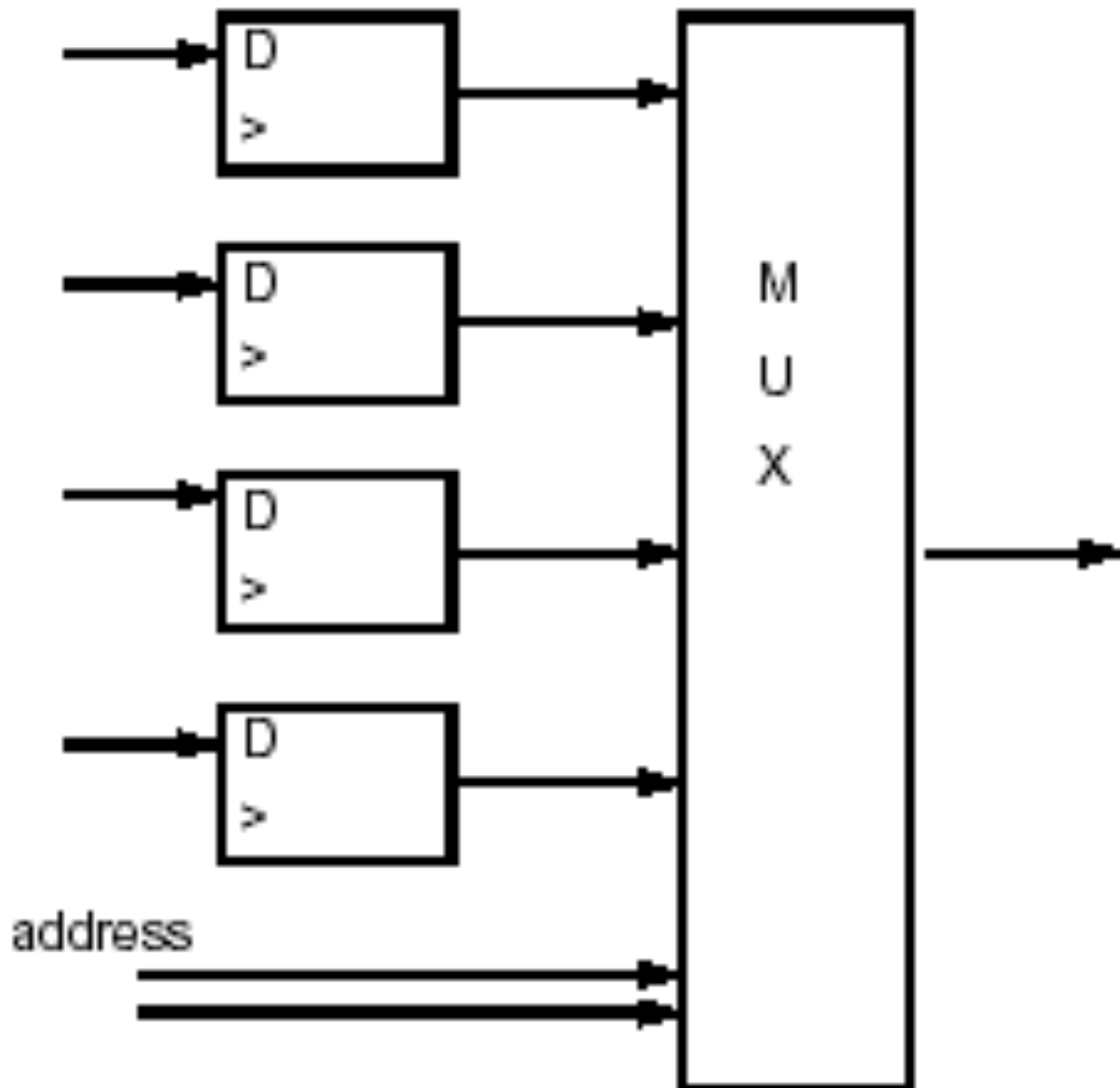


# Write Part

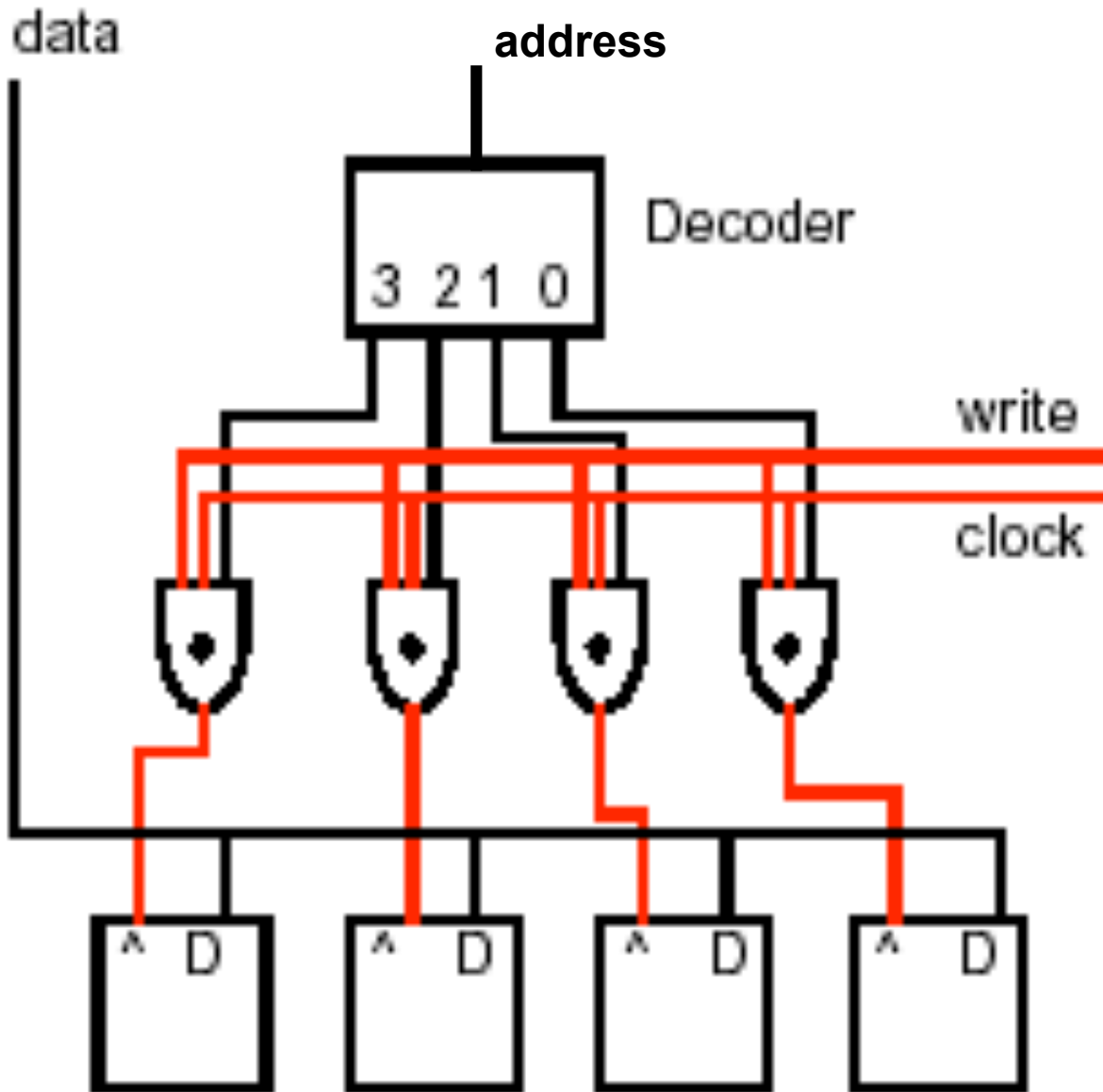


Note the clock input of the flip-flop

# The Whole Thing

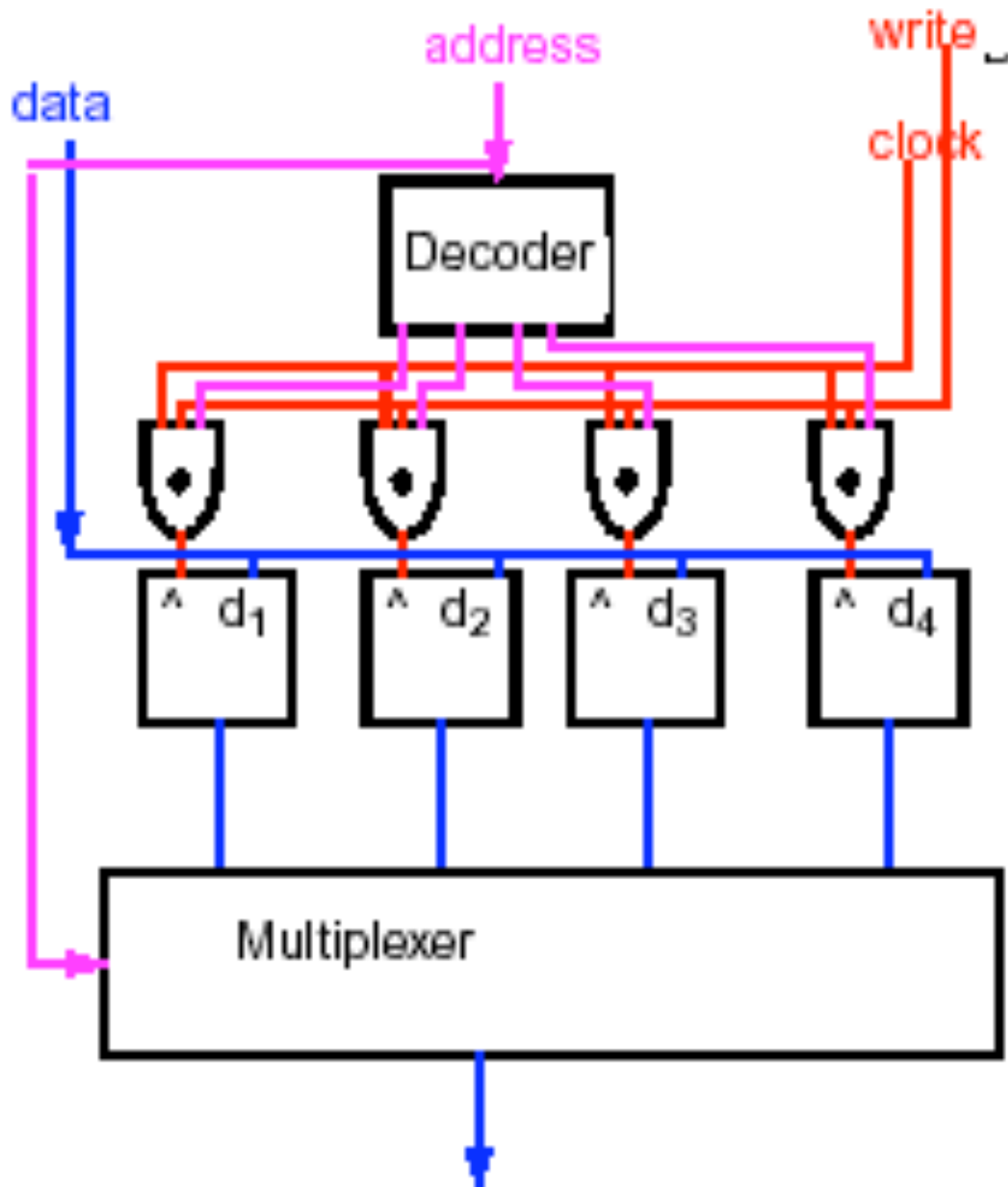

# 1-bit Register File


We want each register storing one bit

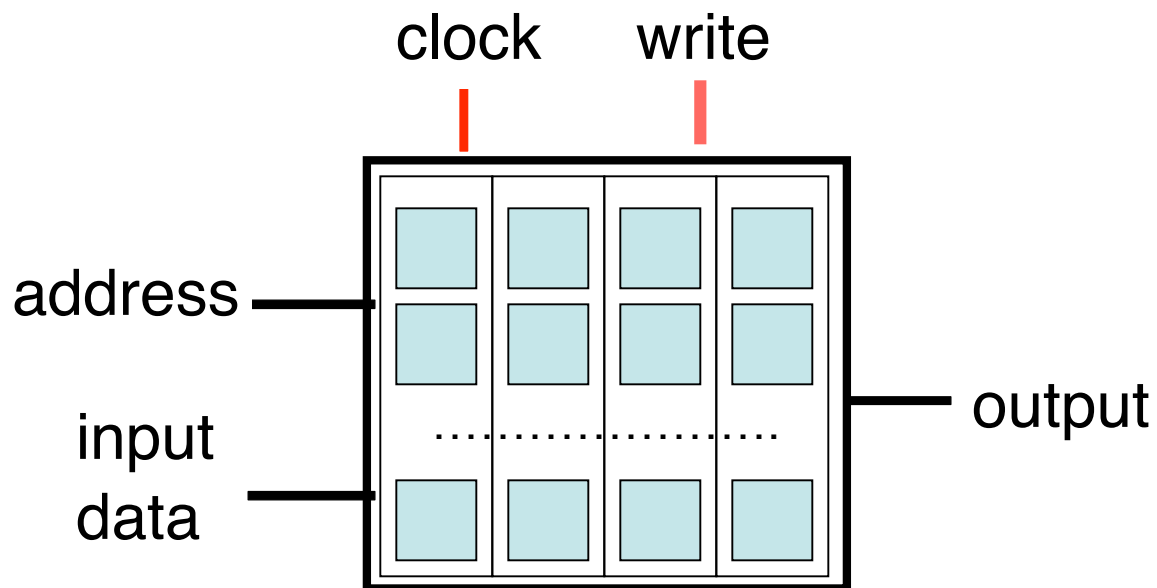


Proceed in two parts

- Read Part
- Write Part

# 8-bit Register File with 4 Registers

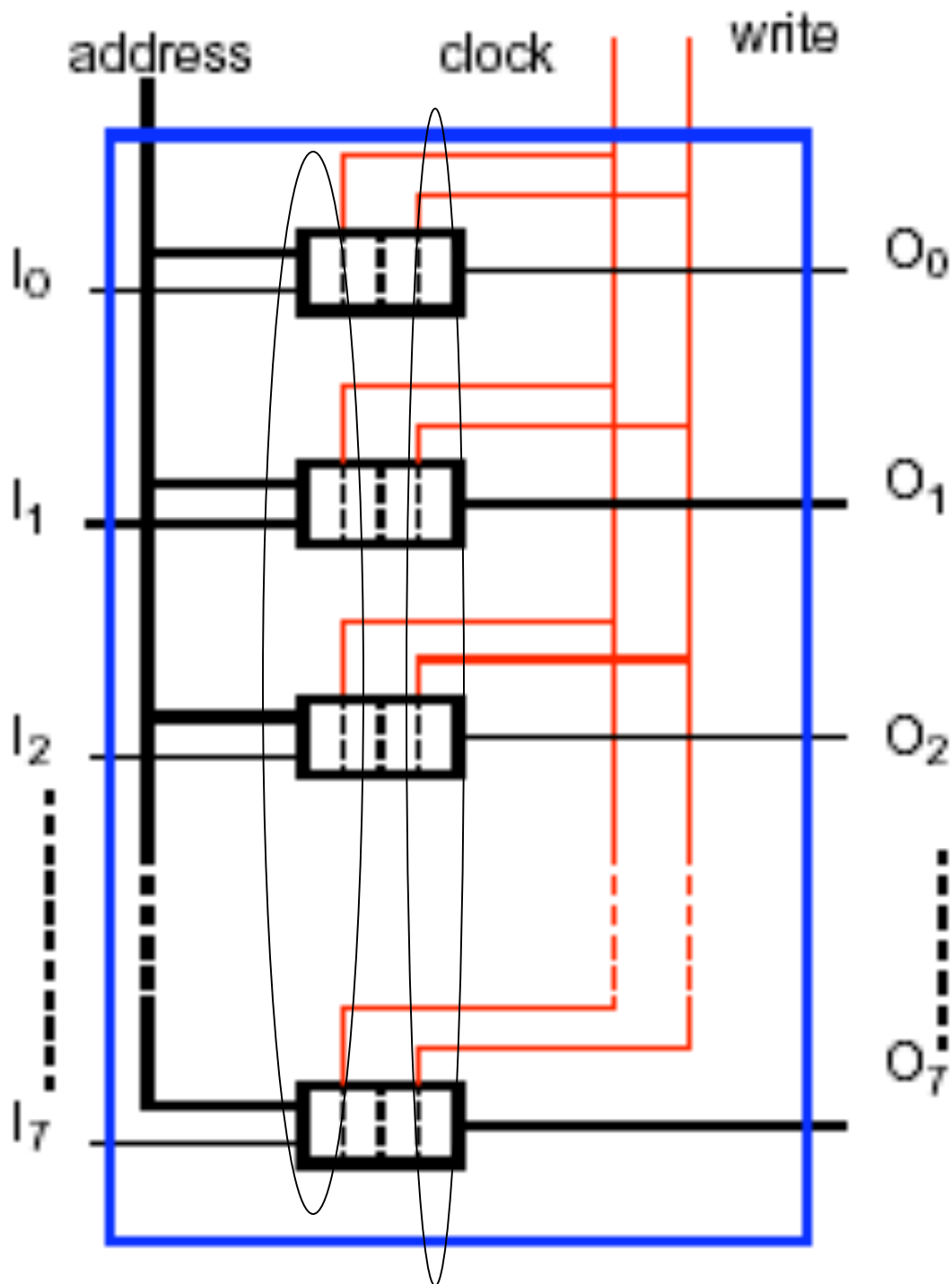

# Bus

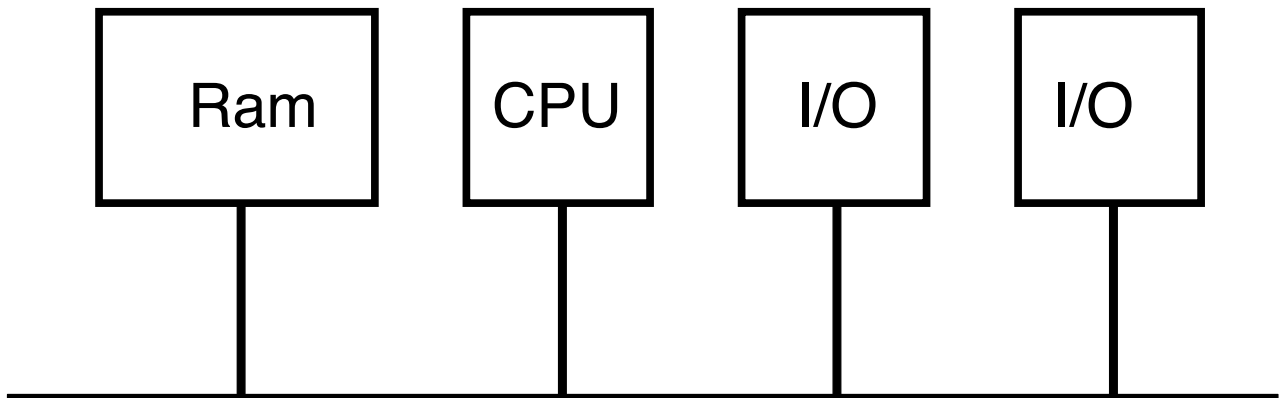

## Motivation

- Many devices need to communicate with each other
- Many wires to connect them all
- A bus is a way to share the wires

## Problem to solve

- Making sure that no two devices write on the bus at the same time


# Tri-state

## Basic Idea: three-states

- 1, 0, high impedance
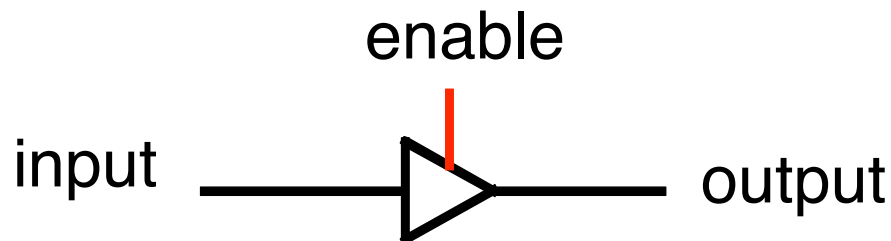
## Behavior

- when enable is asserted, the output is the input
- when enable is deasserted, the output has a high impedance value
- a high impedance value means that the output can be driven by some other device




# High Impedance

When an output is in the high impedance state, it is as though there were no connection

- Think of a very high, essentially infinite, resistance between the power supply, ground lines and the output
- Think of a water pipe
  1. Value 1 is 10 gallons/sec (high)
  2. Value 0 is 2 gallons/sec (low)
  3. High impedance is 0 gallons/sec (off)


# Bus Again

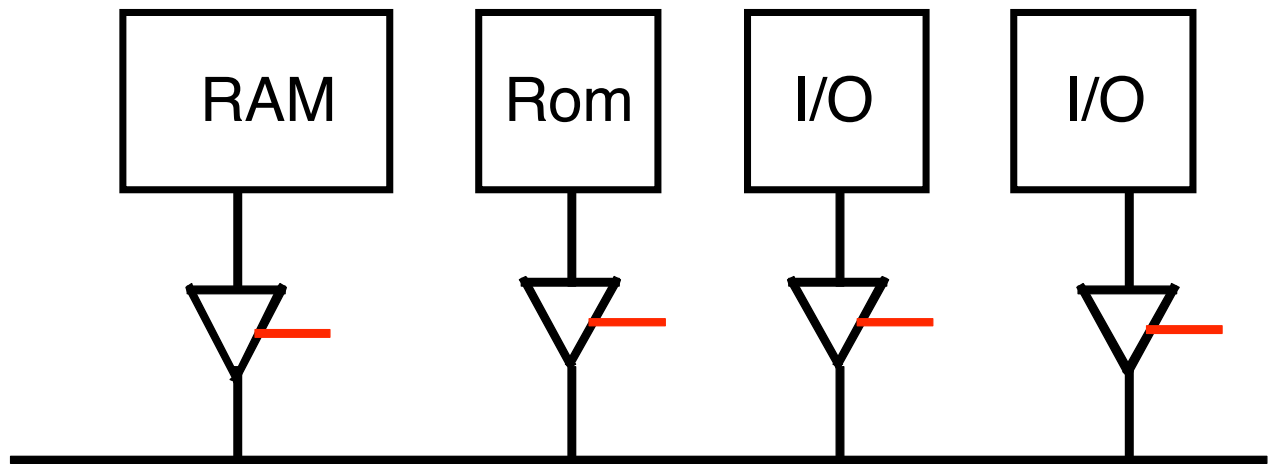

At any time

- only one of the tri-states can be enabled

# RAM

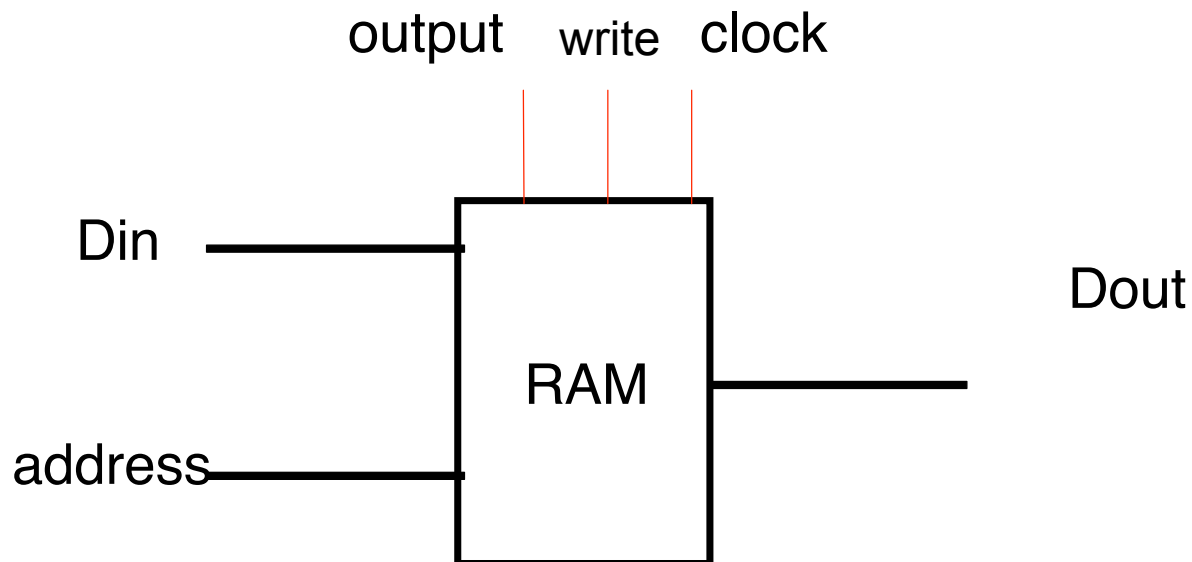


## Control Bits

- Output bit: controls whether the data should be driven on Dout; useful to connect to a bus
- Write bit: controls whether the input should be written at the address

# RAM Implementation

Too large to build a multiplexer

- use tri-states instead

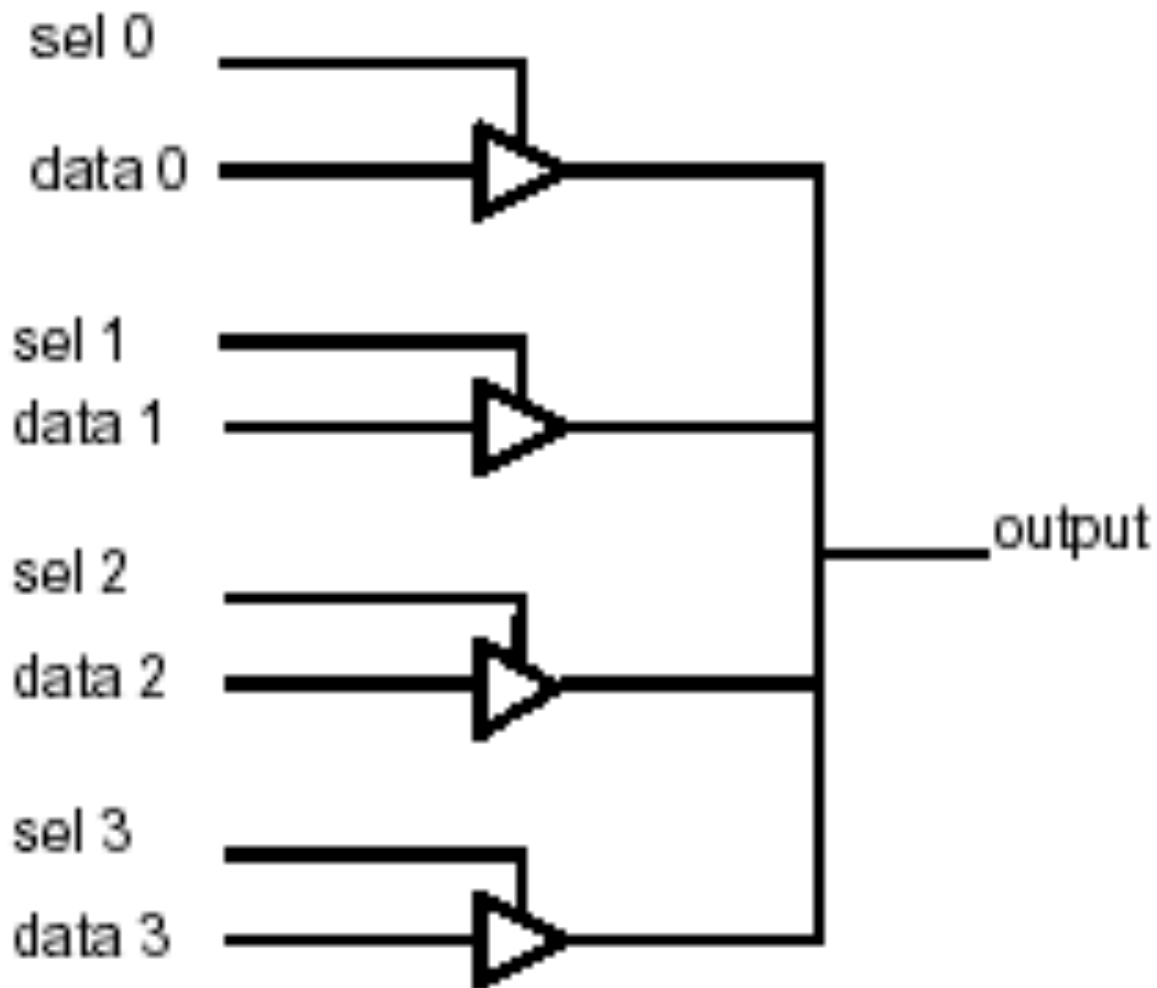

# RAM Implementation


## Basic Idea

- Integrate the tri-state in the flip-flop so that it can be connected to a shared wire
- One shared wire per output
- One Decoder

## Main difference from a register file

- No multiplexer

# RAM/ROM in Diglog

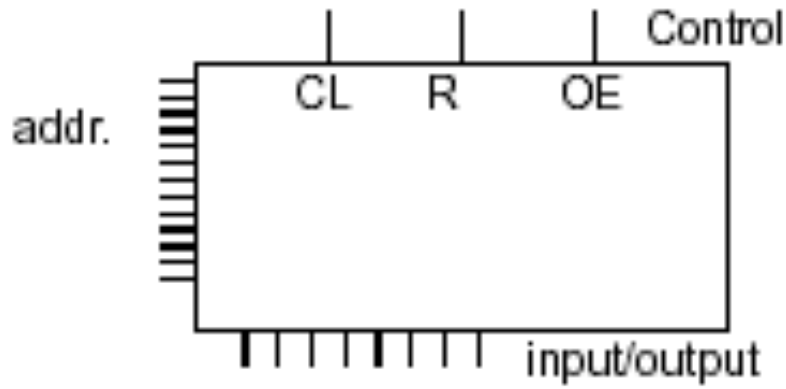

## Basic Feature

- Inputs/Outputs share the same ports

## Basic Control of the RAM/ROM

CL	R	OE	Action
0	1	0	read
0	0	x	write
0	1	1	noop
1	x	x	noop

# The Good News

We have everything we need to  
build a computer now!